



Family name:  
ID:

Name:

| QUESTION | a | b | c |
|----------|---|---|---|
| 1        |   |   |   |
| 2        |   |   |   |
| 3        |   |   |   |
| 4        |   |   |   |
| 5        |   |   |   |
| 6        |   |   |   |
| 7        |   |   |   |
| 8        |   |   |   |
| 9        |   |   |   |
| 10       |   |   |   |

*All the items have been prepared thinking of the field of Industrial Electronic Equipment.  
Correct answer: +1 Wrong answer: -1/3 No answer: 0*

1.- The magnetic coupling between two loops depends on:

- a) the length of the cables
- b) the width of the cables
- c) the loop area


2.- To make a correct PCB design:

- a) Use one power ground for both control and power signals
- b) Keep tracks close to the return
- c) Place all the noisy signals together

3.- Which of the following capacitors has the best connection?




(1)

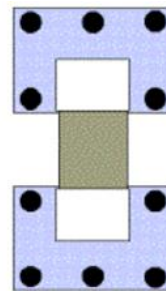

(2)


- a) Connection (1), because it reduces cross-talking
- b) Connection (1), because it increases the series inductance.
- c) Connection (2), because it reduces the series inductance.

4.-To filter common mode currents

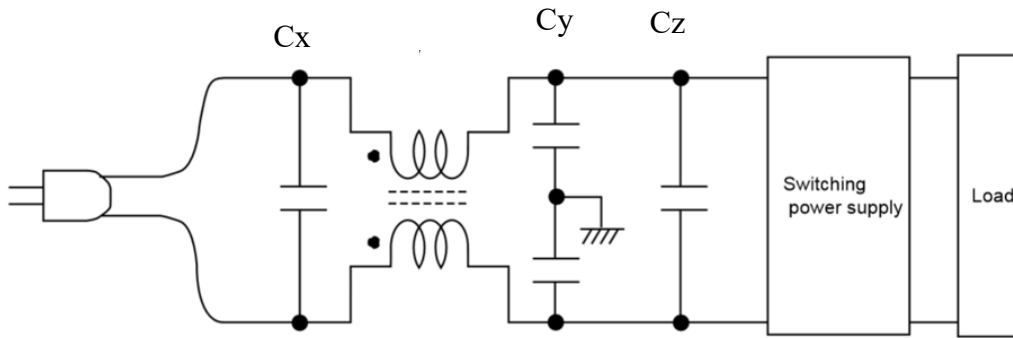


- a) It is necessary to include capacitors  $C_x$  and  $C_z$ .
- b) It is necessary to include capacitor  $C_z$ .
- c) It is necessary to include capacitor  $C_y$ .

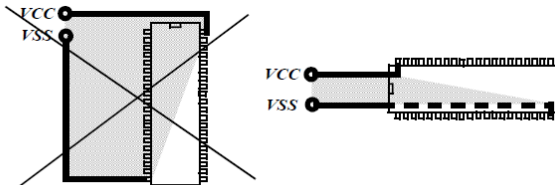5.-The correct tracking minimizes susceptibility problems because




- a) It reduces the length of the tracks.
- b) It increases the parasitic capacitance between tracks.
- c) It reduces the loop defined by the tracks.


6.- Select the correct filter

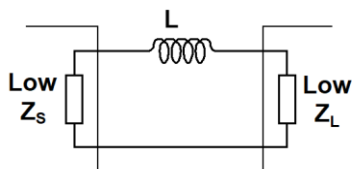

[1]

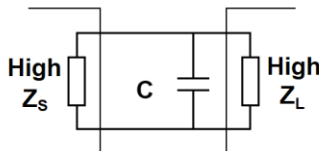

[2]

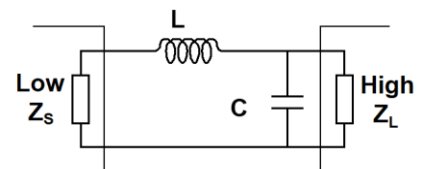

[3]


- a) Filter 1
- b) Filter 2
- c) Filter 3

7.- Noisy differential mode currents can be minimized

- a) with shielding.
- b) with a ground plane.
- c) with ceramic capacitors.

- 8- Noisy common mode currents can be minimized
- a) by avoiding connection of heatsinks to ground.
  - b) with electrolytic capacitors.
  - c) with snubbers.

9.-In the figure

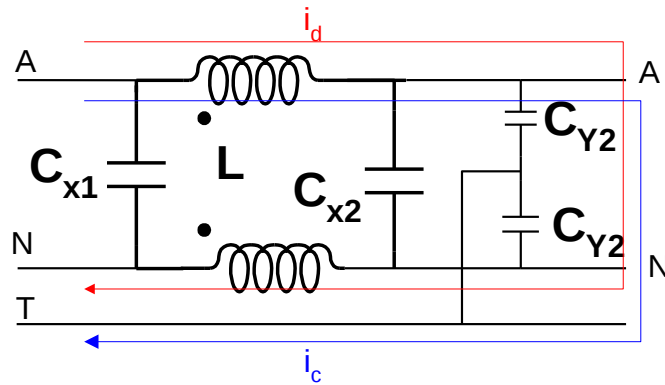

- a)  $C_y$  mainly reduce differential mode currents.
- b)  $C_x$  mainly reduce differential mode currents.
- c)  $L$  mainly reduces differential mode currents.

10.- Select the correct statement

- a) Current amplitude is the most important parameter related to electromagnetic noise.
- a) Do not keep power ground and control ground separately.
- a) Keep tracks close to the return.